

Part A

1. a) Circuit A

$$1. R_T = 20 + 30 + 50 \\ = 100 \Omega$$

$$V = IR$$

$$2. I = \frac{V}{R} = \frac{125}{100} = 1.25 \text{ A}$$

3. Current remains the same

$$4. V = IR$$

$$20 \Omega \rightarrow 1.25 \times 20 = 25 \text{ V}$$

$$30 \Omega \rightarrow 1.25 \times 30 = 37.5 \text{ V}$$

$$50 \Omega \rightarrow 1.25 \times 50 = 62.5 \text{ V}$$

$$5. P = VI$$

$$20 \Omega \rightarrow 25 \times 1.25 = 31.25 \text{ W}$$

$$30 \Omega \rightarrow 37.5 \times 1.25 = 46.88 \text{ W}$$

$$50 \Omega \rightarrow 62.5 \times 1.25 = 78.13 \text{ W}$$

Circuit B

$$1. \frac{1}{R_T} = \frac{1}{20} + \frac{1}{100} + \frac{1}{50} = 0.08 \Omega = \frac{1}{0.08} = 12.5 \Omega$$

$$2. I = \frac{V}{R} = \frac{125}{12.5} = 10 \text{ A}$$

$$3. 20 \Omega \rightarrow \frac{125}{20} = 6.25 \text{ A}$$

$$100 \Omega \rightarrow \frac{125}{100} = 1.25 \text{ A}$$

$$50 \Omega \rightarrow \frac{125}{50} = 2.5 \text{ A}$$

4. Voltage across each resistor is the same

$$(5) P = VI$$

$$20 \Omega \rightarrow 125 \times 6.25 = 781.25 \text{ W}$$

$$100 \Omega \rightarrow 125 \times 1.25 = 156.25 \text{ W}$$

$$50 \Omega \rightarrow 125 \times 2.5 = 312.5 \text{ W}$$